

# Generation and Demodulation of DSB-SC Amplitude Modulated Signals

## 1 Objectives

- Generation of DSB-SC amplitude modulated signals using a diode-based switching modulator circuit.
- Demodulation of the generated AM signal using envelope detector circuit.

## 2 Theory Overview

A double-sideband, suppressed carrier (DSB-SC) AM signal is obtained by multiplying the message signal  $m(t)$  with the carrier signal  $c(t)$ . Thus, we have the amplitude modulated signal [1]

$$s(t) = m(t)c(t) = A_c m(t) \cos(2\pi f_c t). \quad (1)$$

Accordingly, the device used to generate the DSB-SC modulated wave is referred to as a product modulator. We also note that unlike conventional amplitude modulation, DSB-SC modulation is reduced to zero whenever the message signal is switched off.

Also, observe that the modulated signal undergoes a phase reversal whenever the message signal crosses zero, as indicated in Figure 1 for the message signal depicted in part (a) of the figure. The envelope of a DSB-SC modulated signal is therefore different from the message signal, which means that simple demodulation using an envelope detection is not a viable option for DSB-SC modulation.

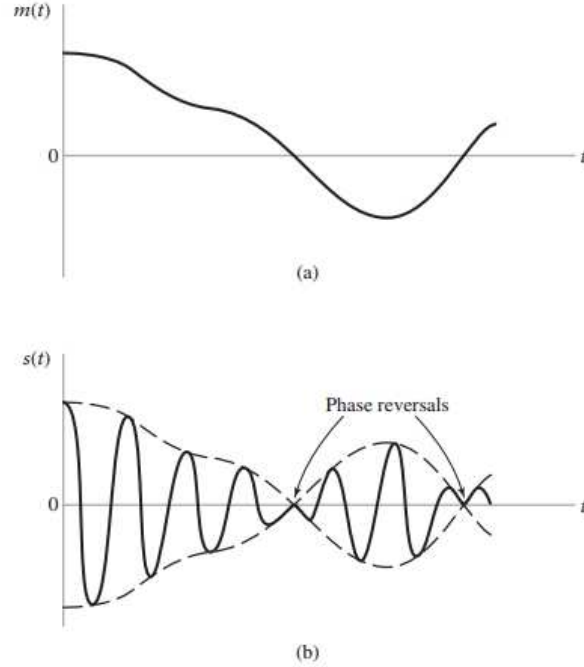


Figure 1: Message signal and DSB-SC modulated wave [1]

### 3 Circuit and Its Working Principle

The product operation needed for the generation of DSB-SC signals (as shown in (1)), is realized with the help of diode-based *switching modulator* circuit. The process of the generation of the DSB-SC signals is depicted in Figure 2. The circuit for the same is shown in Figure 3.

The switching modulator comprises of a diode-bridge having four diodes D1, D2, D3 and D4. The switching of the diodes is controlled by the carrier signal  $c(t)$  [2]. It is also known as Chopper modulator. When the voltage at **A** is greater than that at **B**, all the diodes will be reverse-biased and the amplitude of the message signal will be output. When the voltage at **A** is smaller than that at **B**, then all the four diodes will be forward-biased and then zero-output is obtained. This switching results in the multiplication of the message signal  $m(t)$  with a periodic square wave  $w(t)$  with period equal to the carrier frequency  $f_c$  [3]. Since  $w(t)$  is a periodic square signal with fundamental frequency  $f_c$ , it can be expressed in terms of Fourier series and it contains many harmonics of  $f_c$ . The signal  $m(t)w(t)$  contains infinite number of modulated signals with carrier frequencies  $f_c, 3f_c, 5f_c, \dots$ . However, we are interested only in  $A_c m(t) \cos(2\pi f_c t)$ . In order to extract this component, a band-pass filter is appended to the bridge circuit. The center frequency of the filter should be  $f_c$ .

To apply the envelope detector for the DSB-SC signals, sometimes, a DC offset is added to the modulating signal  $m(t)$ . This ensures that  $m(t) \geq 0$  and the modulated signal  $s(t)$  does not undergo phase reversal. Hence, the message signal can be extracted from the positive envelope ( But the question: Is the carrier suppression maintained? ) Consider a simple envelope detector as shown in Figure 4. Here, the RC value should be greater than  $1/f_c$  but less than  $1/f_m$ .

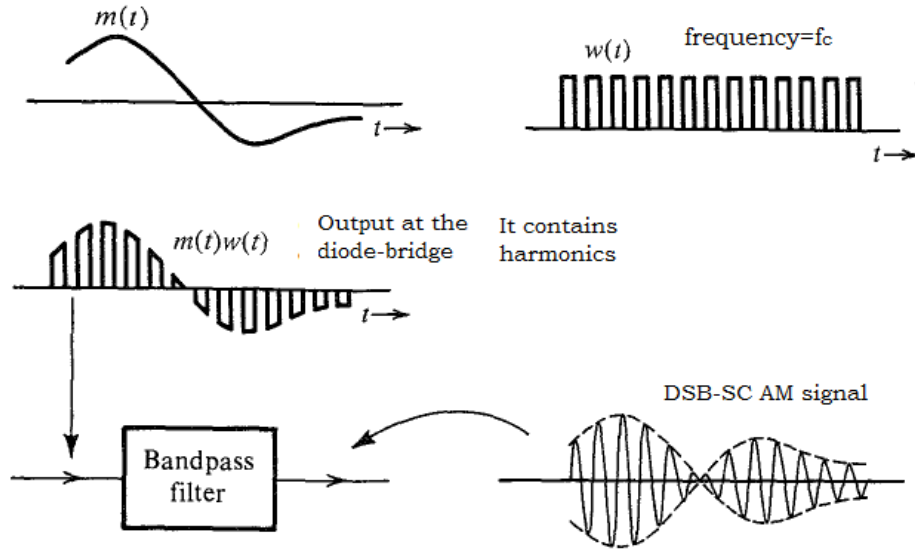


Figure 2: Generation of DSB-SC signals [3]

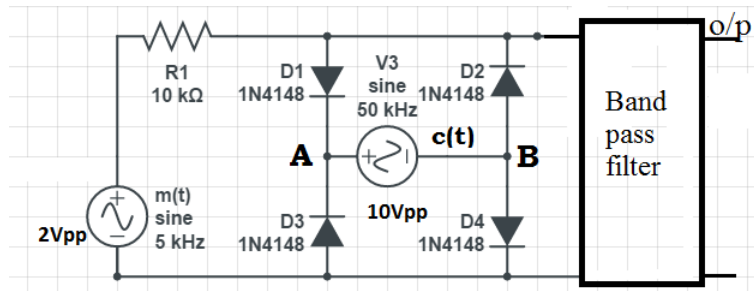


Figure 3: Circuit for generation of DSB-SC signals

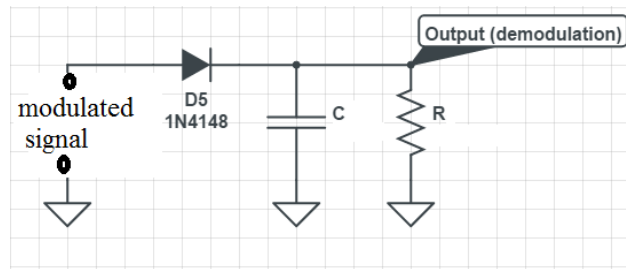


Figure 4: Circuit for Envelope Detector

## 4 Lab Procedures

Perform the following steps:

- Modulation
  - Assemble the circuit as shown in the circuit diagram of Figure 3.
  - Apply a sinusoidal message signal of  $V_{pp}=2V$ ,  $f_m=5$  kHz and a carrier signal of  $V_{pp}=10V$  and  $f_c=50kHz$ .
  - Observe the signal after the diode-based bridge circuit stage.
  - Design the band-pass filter so that the unnecessary harmonics are filtered out.
  - Observe the output of the band-pass filter.
  - Now apply a dc offset of 4V to the message signal. Explain the changes in the output of the band-pass filter.
- Demodulation
  - Design the envelope detector circuit in Figure 4 which is to be connected in cascade to the circuit in Figure 3.
  - Measure the output across the resistor R.
  - Observe the waveform carefully. It should be a scaled form of the input modulating signal if the demodulation has been accurate.

### Questions

1. What is the modulation index? Does it depend on the offset value of the message/modulating signal?
2. Explain the switching of the diodes.
3. Write down the challenges faced in the experiment if any and the ways to resolve those issues.

## References

- [1] Haykin and Moher, *An Introduction to Analog and Digital Communications*, (Wiley, Second edition 2012).
- [2] Proakis and Salehi, *Communication System Engineering*, (2nd edition, Prentice Hall, 2003).
- [3] B.P Lathi and Zhi Ding, *Modern Digital And Analog Communication Systems*, (Oxford University Press, Fourth edition 2017).